

TESTING

//Add screenshots here

i. The first limiter circuit reduces peak voltage showing the behavior of the exponential diodes. This makes the output wave more square than the input wave because it is limiting the input before it can start curving back down. The second limiter circuit (find picture to compare)

ii.

iii.

iv. You should be able to make the output signal the same by staying in the region where both diodes are in an "off" state. This will cause the circuit to not be limited by current through the diodes.