



UNIVERSITY OF WASHINGTON

BEE331 LAB 1.2

<i>2301991</i>	<i>1900585</i>
<i>Jason Truong</i>	<i>Henry Haight</i>

supervised by
Prof. Joseph DECUIR

July 15, 2024

Characterising Diodes; I-V Curve

Design Objective

In this lab, we introduce ourselves to the *Zener* diode, we characterise its function by the I-V curve.



Circuit Design Outline

With a resistor of an arbitrary impedance greater than 100Ω ($R \geq 100\Omega$), and the natural impedance of the Function Generator in series ($R_{TOT} = R_{FG} + R \geq 150\Omega$), the (1N4732 or 1n5223) Zener diode is set in series set in reverse-polarity to proccate reverse-breakdown from the diode; through the function generator. Set the function generator @ $f=1\text{kHz}$ and $V_P = 5V$ (We'll be focusing on the negative portion of V_P).


Figure 1: Series R + Diode D_Z

(a) LTSpice + Rudimentary Schematic Seris RD (499 Ω) Circuit

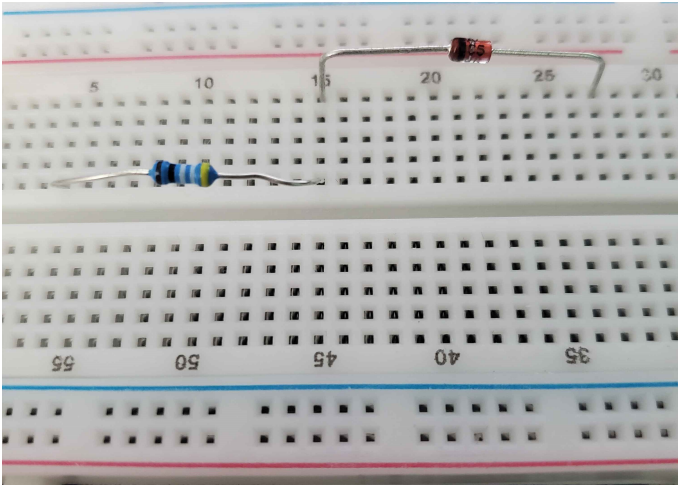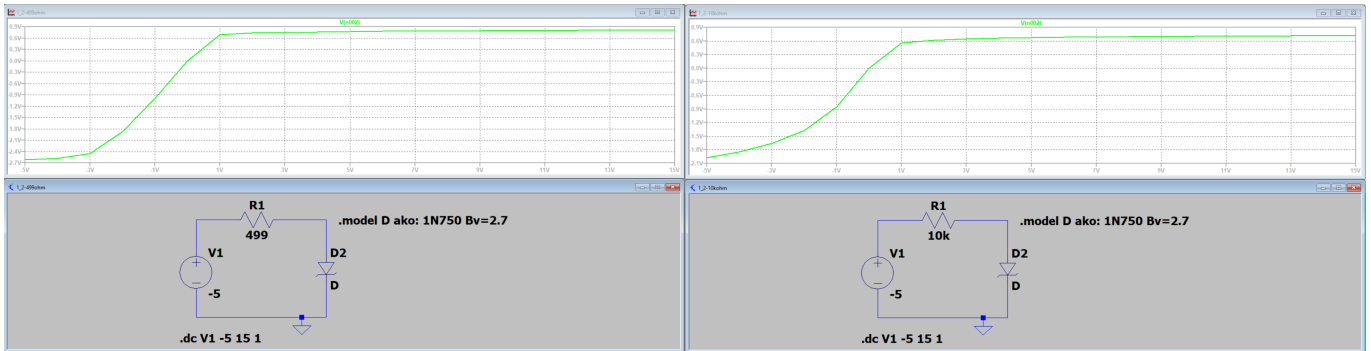(b) LTSpice + Rudimentary Schematic Seris RD (10k Ω) Circuit



(c) Series RD Circuit 499 Ω

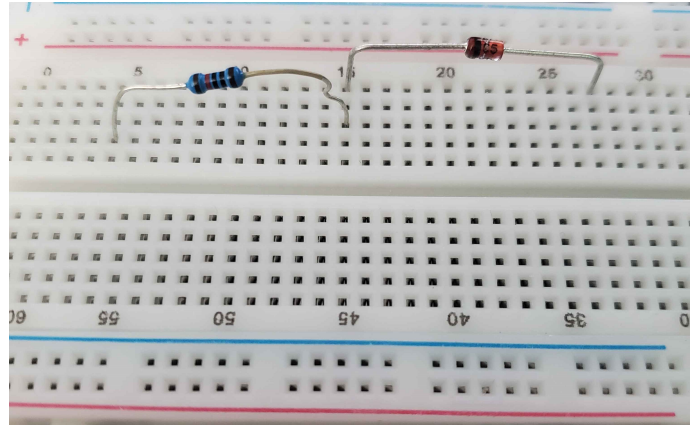


(d) Series RD Circuit 10k Ω

Descriptions of Measurements & Calculations

Given the default theoretical calculation for a Diode in forward-bias: $I_D = I_S(e^{\frac{V_D}{V_T}} - 1)$; the dataset is similar in-nature - not exact because the characteristics of this diode differs - from section 1.1 of the lab.

The characteristic of a *Zener* Diode is its relationship to $-V_D$, as I_D enters **Reverse-Breakdown** @ $-V_{D0}$; the point of breakdown.

Figure 1: RD_Z Circuit

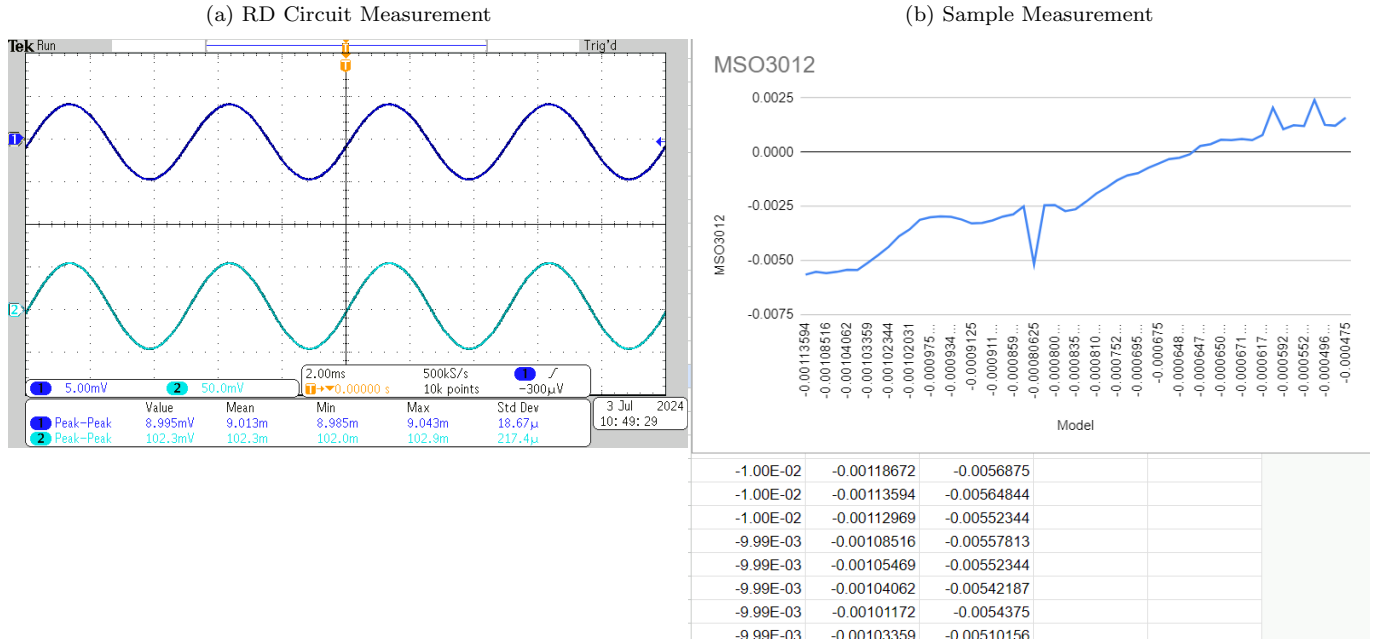

Summary & Conclusions

Revealed in Figure RD-Circuit 1A & 1B, the generated oscilloscope readings of the two periodic function match the characteristics of the transfer function found in 1b (RD_Z Circuit). So the measurements do infact closely align.

Discussion

- i. Describe how you measured I_D and V_D ?

At the node where R; ($R > 100\Omega$) and the Zener Diode; (D_Z) meet, we denote this junction as V_{out} . We attach our Multimetre's positive lead (Red) to V_{out} , and attached our ground lead to the opposing node of the Zener Diode; (D_Z) - which should be grounded.

- ii. In this experiment how would you determine the value of $I_{D,max}$

Forward-Bias: $I_D = I_S(e^{\frac{V_D}{V_T}} - 1)$; reference Figure 1b.

Reverse-Breakdown: The functioning range when $V_D < V_{D_{BR}}$; the output voltage of a reverse-breakdown Zener diode is $V_o = V_i - R_i * i_i$ (the subscript of i meaning input of the function generator.)

- iii. In the circuit, what limits I_D ?

Forward-Bias: The characteristics of the I-V curve of a diode has current I_D exponentially rise towards a cut-off at the threshold, towards the C.V.D @ V_D .

Reverse-Breakdown: Similarly to how the Forward-Bias meets an exponential curve towards its threshold; V_D , the Reverse-Breakdown meets a sharp declination of V_o towards $-V_{D_{BR}}$.

- iv. Explain why V_D does not change much while I_D can change a lot.

Given the equation of a Diode's characteristics of $I_D = I_S(e^{\frac{V_D}{V_T}} - 1)$. Putting the equation in reference to I_D is an exponential function, while V_D is a logarithmic function with a very slow rise time. This goes for both Forward-Bias and Reverse-Breakdown, only the output voltage nature changes.

Bibliography

Cited:

- Lab 1 Manual
- Sedra, Adel, and Kenneth Smith. Microelectronic Circuits. S.L., Oxford Univ Press Us, 2019.
- “How Do You Calculate, a Silicon Junction Diode with $N = 1$ Has $v = 0.7$ v al $I = 1$ MA. What Is the Voltage Drop at $I=0.1$ MA and $I=10$ MA.?” Quora, 2024, appliedmathematics.quora.com/How-to-calculate-A-silicon-junction-diode-with-n-1-has-v-0-7-V-al-I-1-mA-What-is-the-voltage-drop-at-I-0-1-mA-an?top_ans=223007030. Accessed 15 July 2024.



(a) Look at her, she's perfect.