



UNIVERSITY OF WASHINGTON

BEE331 LAB 1.2

<i>2301991</i>	<i>1900585</i>
<i>Jason Truong</i>	<i>Henry Haight</i>

supervised by  
Prof. Joseph DECUIR

July 15, 2024

# Full-Wave Bridge Rectifier Circuit

## Design Objective


In this lab, we introduce ourselves to two voltage rectifying circuits: The Rectifier and Voltage Clamp. We demonstrated this two two applications across 3 circuits. We characterize its function in  $V_{out}$ .

## Circuit Design Outline


[Guidelines do not ask for explanation on design. See Below.]

Figure 1: Bridge Rectifier Circuits

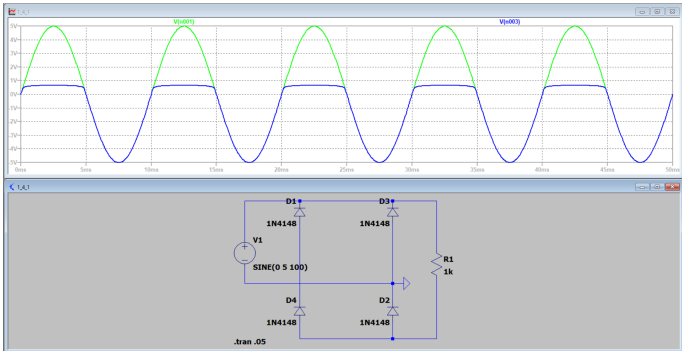(a) LTSpice + Rudimentary Schematic Full-Wave Bridge Rectifier



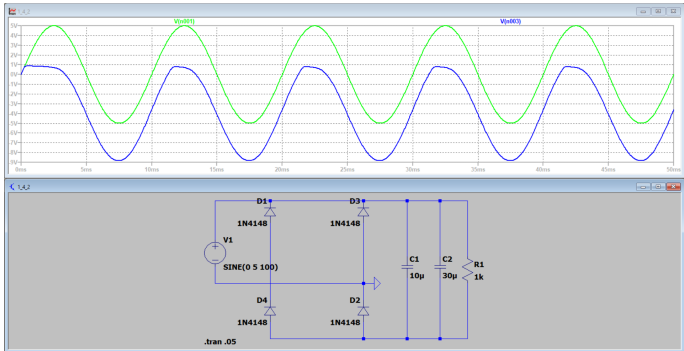(b) LTSpice + Rudimentary Schematic Full-Wave Bridge Rectifier with output filter



(c) LTSpice + Rudimentary Schematic Full-Wave Bridge Rectifier with output filter and Zener diode regulator as its output



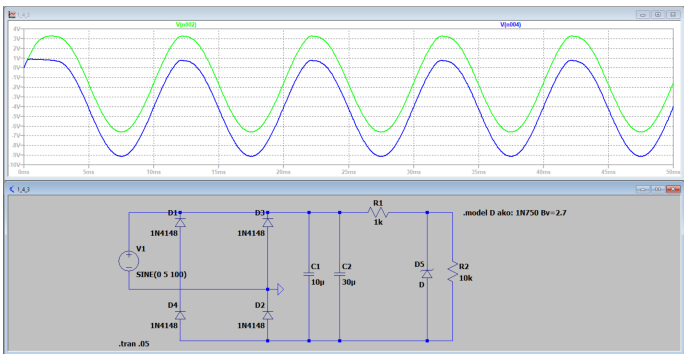


Figure 2: Bridge Rectifier Circuits IRL

(a) Full-Wave Bridge Rectifier

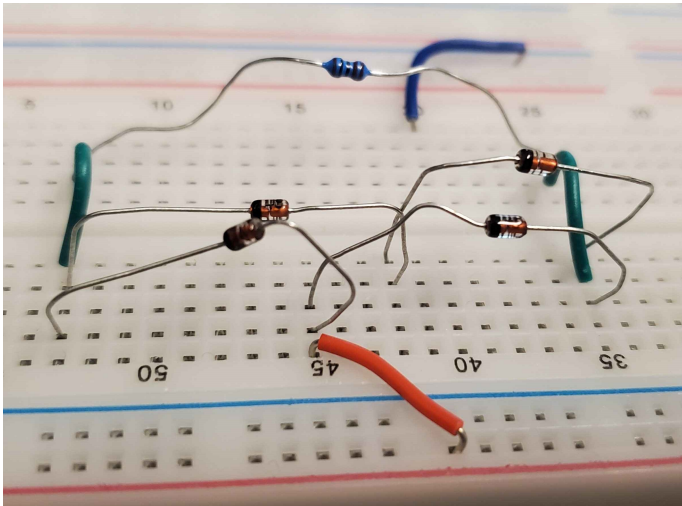

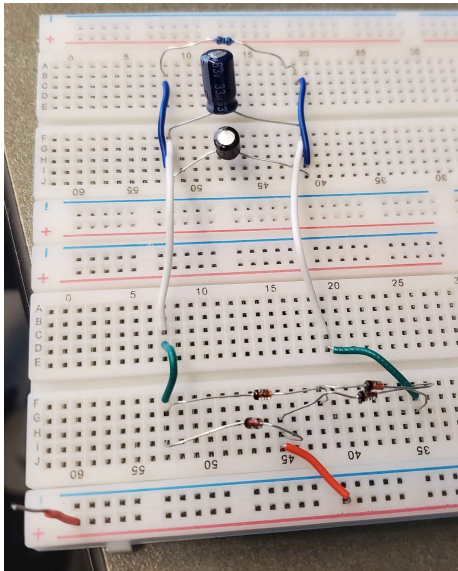(b) LTSpice + Rudimentary Schematic Full-Wave Bridge Rectifier with output filter and Zener diode regulator as its output




## Descriptions of Measurements & Calculations

Given the default theoretical calculation for a Diode in forward-bias:  $I_D = I_S(e^{\frac{V_D}{V_T}} - 1)$ ; the dataset is similar in-nature - not exact because the characteristics of this diode differs - from section 1.1 of the lab.

The characteristic of a *Zener* Diode is its relationship to  $-V_D$ , as  $I_D$  enters **Reverse-Breakdown** @  $-V_{Z0}$ ; the point of breakdown. The utilisation of the Capacitors in the Bridge Circuit is to dissipate the voltage curve over a gentler duration. Because of these characteristics, the Bridge Circuit essentially dampens and *Rectifies* the entering voltage;  $V_{in}$  to  $V_o$

Figure 3: Bridge Rectifier Circuits Scope

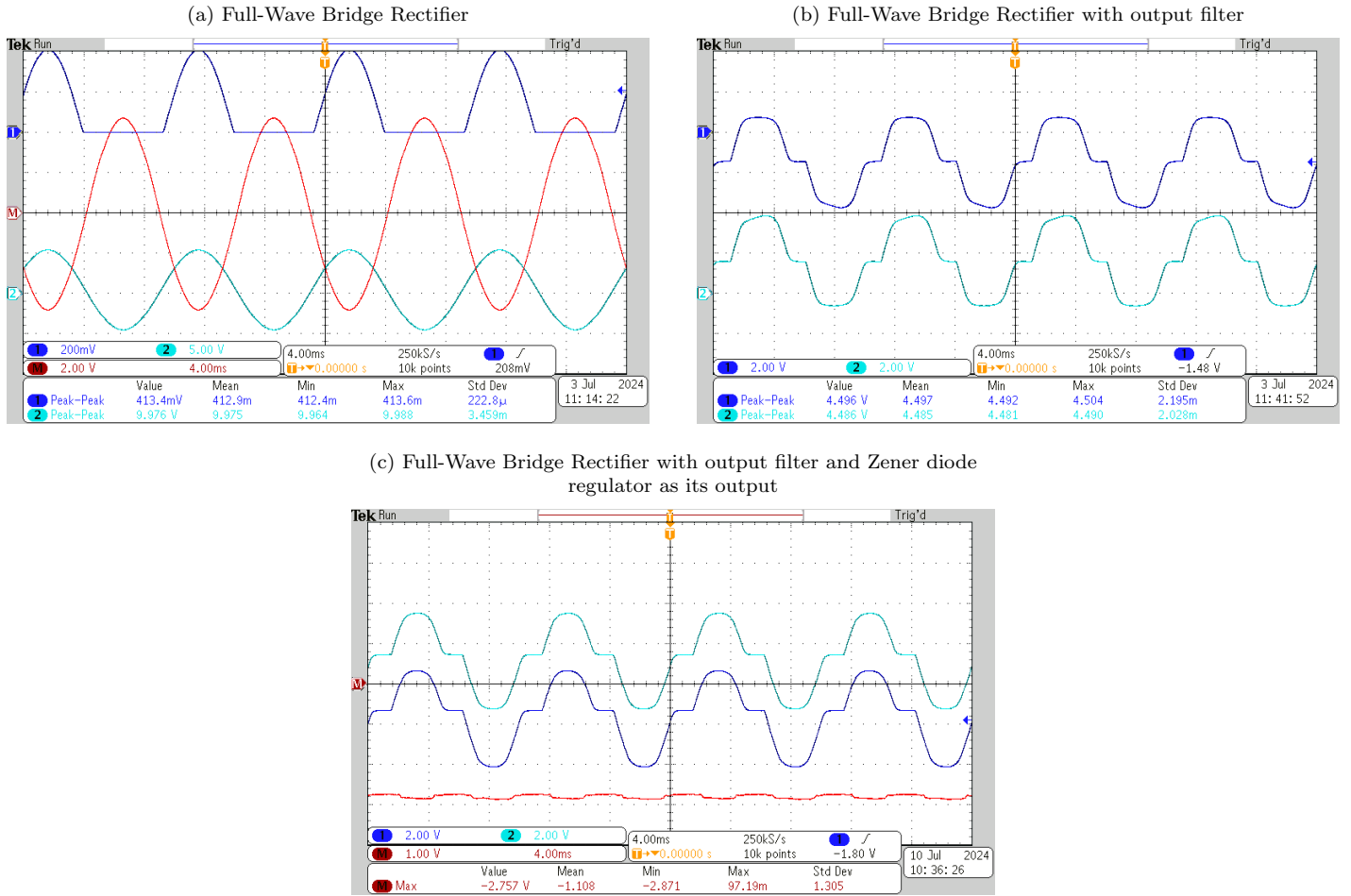

## Summary & Conclusions

Revealed in Figure RDD-Circuit 0A & 0B, the generated oscilloscope readings of the two periodic function do in-fact dampen @  $V_{in}$  (CH2) greatly to  $V_{out}$  (CH1). It is similiary in the Series  $D_Z$  circuit.

## Discussion

- i. Compare the measured versus simulated data and explain any differences.

The measured and simulated data find differences in components, breakdown region, ideal components; which differs in threshold ranges and dampening ranges, and a consistent AC signal that has no attenuation.

- ii. What are the purposes of experiment 1.41, 1.42, and 1.43? You can explain this by comparing the output voltage waveforms.

The purpose of 1.4.1 is to limit the negative values of the AC waveform. The output voltage had no voltage under 0. The purpose of 1.4.2 is to have the circuit charge the capacitors at the turn-on voltage for the diodes then when the input is low enough the capacitor will discharge slowly creating a more linear signal.

- Is it desirable to reduce the output ripple voltage? Why do you think that is?

Signal alignment; although, we would have to consider using a secondary signal system to propagate the missing values - we'd have a consistently voltage running at a timer rate scaling with total Impedances and Voltage output.

It could also be desirable to reduce the output voltage of the ripple because the output voltage might be used for other components that need a certain voltage to operate. So, the ripple voltage can be changed to meet those needs.

- At what load resistance does the regulated full-wave bridge rectifier come out of regulation?

$$R_{Load} \geq 1k\Omega$$

- Explain how you would predict the minimum value of the load resistance for which the Zener diode still operates in the breakdown region.

Deriving the theoretical calculation of the Zener Diode's breakdown range;  $V_o = V_i - R_i * i$  @  $D_{ZBR}$ , and considering  $R_{Load} \geq (R_2 * \epsilon)$ .

## Bibliography

### Cited:

- Lab 1 Manual
- Sedra, Adel, and Kenneth Smith. Microelectronic Circuits. S.L., Oxford Univ Press Us, 2019.
- “How Do You Calculate, a Silicon Junction Diode with  $N = 1$  Has  $v = 0.7$  v al  $I = 1$  MA. What Is the Voltage Drop at  $I=0.1$  MA and  $I=10$  MA.?” Quora, 2024, [appliedmathematics.quora.com/How-to-calculate-A-silicon-junction-diode-with-n-1-has-v-0-7-V-al-I-1-mA-What-is-the-voltage-drop-at-I-0-1-mA-an?top\\_ans=223007030](https://appliedmathematics.quora.com/How-to-calculate-A-silicon-junction-diode-with-n-1-has-v-0-7-V-al-I-1-mA-What-is-the-voltage-drop-at-I-0-1-mA-an?top_ans=223007030). Accessed 15 July 2024.



(a) Look at her, she's perfect.